

CS6846 – Quantum Algorithms and Cryptography


Going beyond Classical



Instructor: Shweta Agrawal, IIT Madras
Email: shweta@cse.iitm.ac.in


CCNOT or Toffoli Gate

 Recall the definition of fanin and fanout



CCNOT or Toffoli Gate

 
Recall the definition of fanin and fanout




Claim: Toffoli gate can be used to simulate fanout

CCNOT or Toffoli Gate

 Recall the definition of fanin and fanout



 Claim: Toffoli gate can be used to simulate fanout




Contradiction to No Cloning?

No.



Having fun with circuits

 What state does the following circuit construct?



$$|\phi\rangle = H|0\rangle \otimes |0\rangle = |+\rangle|0\rangle = \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle)|0\rangle$$

$$\begin{aligned} |\psi\rangle &= \text{CNOT} \left(\frac{1}{\sqrt{2}} |00\rangle + |10\rangle \right) \\ &= \frac{1}{\sqrt{2}} (|00\rangle + |11\rangle) \quad \text{EPR state} \end{aligned}$$

Having fun with EPR

$$\text{EPR} = \frac{1}{\sqrt{2}} (|00\rangle + |11\rangle)$$

We pass through $H \otimes H$, i.e. apply H to each qubit.

$$H \otimes H \left(\frac{1}{\sqrt{2}} (|00\rangle + |11\rangle) \right) = \frac{1}{\sqrt{2}} (|+\rangle|+\rangle) + \frac{1}{\sqrt{2}} (|-\rangle|-\rangle)$$

$$= \frac{1}{\sqrt{2}} \left(\frac{1}{\sqrt{2}} |0\rangle + \frac{1}{\sqrt{2}} |1\rangle \right) \left(\frac{1}{\sqrt{2}} |0\rangle + \frac{1}{\sqrt{2}} |1\rangle \right) +$$

$$\frac{1}{\sqrt{2}} \left(\frac{1}{\sqrt{2}} |0\rangle - \frac{1}{\sqrt{2}} |1\rangle \right) \left(\frac{1}{\sqrt{2}} |0\rangle - \frac{1}{\sqrt{2}} |1\rangle \right)$$

$$= \frac{1}{2\sqrt{2}} |00\rangle + \cancel{\frac{1}{2\sqrt{2}} |01\rangle} + \cancel{\frac{1}{2\sqrt{2}} |10\rangle} + \frac{1}{2\sqrt{2}} |11\rangle$$

$$+ \frac{1}{2\sqrt{2}} |00\rangle - \cancel{\frac{1}{2\sqrt{2}} |01\rangle} - \cancel{\frac{1}{2\sqrt{2}} |10\rangle} + \frac{1}{2\sqrt{2}} |11\rangle$$

$$= \frac{1}{\sqrt{2}} |00\rangle + \frac{1}{\sqrt{2}} |11\rangle.$$

Capturing Classical Computation

- **Want:** Given classical $f : \{0, 1\}^n \rightarrow \{0, 1\}$, want to evaluate using quantum system.

Capturing Classical Computation

- **Want:** Given classical $f : \{0, 1\}^n \rightarrow \{0, 1\}$, want to evaluate using quantum system.
- **Want:** A unitary U such that $\underline{U|x\rangle} = \underline{|f(x)\rangle}$.


Capturing Classical Computation

- **Want:** Given classical $f : \{0, 1\}^n \rightarrow \{0, 1\}$, want to evaluate using quantum system.
- **Want:** A unitary U such that $U|x\rangle = |f(x)\rangle$.
- **Note:** f must be bijective for such a unitary to exist.

Capturing Classical Computation

- **Want:** Given classical $f : \{0, 1\}^n \rightarrow \{0, 1\}$, want to evaluate using quantum system.
- **Want:** A unitary U such that $U|x\rangle = |f(x)\rangle$.
- **Note:** f must be bijective for such a unitary to exist.

 If f is bijective, the computation can be reversed.



Reversible Computation

Reversible Gates

A Boolean gate G is said to be reversible if it has the same number of inputs as outputs, and its mapping from input strings to output strings is a bijection.


Reversible Computation

Reversible Gates

A Boolean gate G is said to be reversible if it has the same number of inputs as outputs, and its mapping from input strings to output strings is a bijection.

Reversible circuits can be implemented by unitary transformations – to reverse computation, run the circuit in inverse (or apply inverse of unitary).

Reversible Computation

 

Input	Output
$ 000\rangle$	$ 000\rangle$
$ 001\rangle$	$ 001\rangle$
$ 010\rangle$	$ 010\rangle$
$ 011\rangle$	$ 011\rangle$
$ 100\rangle$	$ 100\rangle$
$ 101\rangle$	$ 101\rangle$
$ 110\rangle$	$ 111\rangle$
$ 111\rangle$	$ 110\rangle$

Figure: The CCNOT (Toffoli) Gate is reversible implementation of NAND

Reversing Arbitrary Circuits

NAND gates are universal for classical computing.



1) Eliminate OR.

DeMorgan's law:
$$\text{OR}(x_1, x_2) = \text{NOT}(\text{AND}(\text{NOT}(x_1), \text{NOT}(x_2)))$$

2) Eliminate AND
$$\text{AND} = \text{NOT}(\text{NAND})$$

3) Eliminate NOT.

$$\text{NOT}(x) = \text{NAND}(x, 1)$$

  

Uncomputing: Clean up ancillary bits

Consider circuit:

$$|x\rangle \otimes |0\rangle^{\otimes k} \otimes |0\rangle \longmapsto |x\rangle \otimes |0\rangle^{\otimes k} \otimes |\text{output}\rangle$$

Uncomputing: Clean up ancillary bits

Consider circuit:

$$|x\rangle \otimes |0\rangle^{\otimes k} \otimes |0\rangle \longmapsto |x\rangle \otimes |0\rangle^{\otimes k} \otimes |\text{output}\rangle$$

Uncompute $|0\rangle^{\otimes k}$ to “refresh” back to zeroes.

Uncomputing: Clean up ancillary bits

Consider circuit:

$$f: \{0, 1\}^n \rightarrow \{0, 1\}.$$

$$|x\rangle \otimes |0\rangle^{\otimes k} \otimes |0\rangle \mapsto |x\rangle \otimes |0\rangle^{\otimes k} \otimes |\text{output}\rangle$$

Uncompute $|0\rangle^{\otimes k}$ to “refresh” back to zeroes.

 


Figure: A Quantum Circuit that Uses Uncomputing

Uncomputing: Clean up ancillary bits

Consider circuit:

$$|x\rangle \otimes |0\rangle^{\otimes k} \otimes |0\rangle \mapsto |x\rangle \otimes |0\rangle^{\otimes k} \otimes |\text{output}\rangle$$

Uncompute $|0\rangle^{\otimes k}$ to “refresh” back to zeroes.

 


Figure: A Quantum Circuit that Uses Uncomputing

Can write circuit as $|x\rangle \otimes |0\rangle \mapsto |x\rangle \otimes |\text{output}\rangle$

Now we can compute...

Implementing Classical Functions

A quantum circuit C_f implements a classical function $f : \{0, 1\}^n \mapsto \{0, 1\}^m$ if $\forall x \in \{0, 1\}^n, \forall y \in \{0, 1\}^m,$

$$C_f(|x\rangle |y\rangle \underline{|0\rangle^{\otimes k}}) \mapsto (|x\rangle |y \oplus \underline{f(x)}\rangle \underline{|0\rangle^{\otimes k}})$$

Now we can compute...

Implementing Classical Functions


A quantum circuit C_f implements a classical function $f : \{0, 1\}^n \mapsto \{0, 1\}^m$ if $\forall x \in \{0, 1\}^n, \forall y \in \{0, 1\}^m$,

$$C_f(|x\rangle |y\rangle |0\rangle^{\otimes k}) \mapsto (|x\rangle |y \oplus f(x)\rangle |0\rangle^{\otimes k})$$

As mentioned, the ancillary qubits will be usually omitted and the transformation can be rewritten as $C_f(|x\rangle |y\rangle) \mapsto (|x\rangle |y \oplus f(x)\rangle)$

Classical Computation

 - Claim: Can compute any deterministic classical circuit!



Classical Computation

- Claim: Can compute any randomized circuit!!

As we saw, [?]_o can generate true randomness by using Hadamard basis states measured using classical basis.

Universal Gates for Quantum Computation

Can Toffoli be a universal gate for quantum computation?

Universal Gates for Quantum Computation

Can Toffoli be a universal gate for quantum computation?

Ans: No, just a permutation matrix. Cannot even implement Hadamard Transform.

Universal Gates for Quantum Computation

Can Toffoli be a universal gate for quantum computation?

Ans: No, just a permutation matrix. Cannot even implement Hadamard Transform.

Can {Toffoli, H} be universal gates for quantum computation?

Universal Gates for Quantum Computation

Can Toffoli be a universal gate for quantum computation?

Ans: No, just a permutation matrix. Cannot even implement Hadamard Transform.

Can {Toffoli, H} be universal gates for quantum computation?

Ans: No, these map real vectors to only real vectors so how could phase shifts and other complex transformations be supported?

Universal Gates for Quantum Computation

Can Toffoli be a universal gate for quantum computation?

Ans: No, just a permutation matrix. Cannot even implement Hadamard Transform.

Can {Toffoli, H} be universal gates for quantum computation?

Ans: No, these map real vectors to only real vectors so how could phase shifts and other complex transformations be supported?

Universal Quantum Gates

The set {Toffoli(or CNOT), H , $\begin{bmatrix} 1, 0 \\ 0, e^{i\pi/4} \end{bmatrix}$ } is quantum universal.

Quantum Parallelism

Ok, first let us see how to generate superposition of function inputs.

Apply $H^{\otimes 2}$ to $(|0\rangle, |0\rangle)$.



$$\begin{aligned} |1\rangle|1\rangle &= \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \\ &= \frac{1}{2}(|00\rangle + |01\rangle + |10\rangle + |11\rangle) \end{aligned}$$


Generalize to n bits?

$$H^{\otimes n}(|0\rangle^n) = \frac{1}{2^{n/2}} \sum_{x \in \{0,1\}^n} |x\rangle.$$

Quantum Parallelism


Now let us see how to generate superposition of function *outputs*.

Single bit:

 

$$\phi = \frac{1}{\sqrt{2}} (|0\rangle|0\rangle + |1\rangle|0\rangle)$$

showed

 

if $x = |0\rangle$, we get (on 2nd wire) $y \oplus |f(0)\rangle$. if $y = |0\rangle$, get $|f(0)\rangle$.

if $x = |1\rangle$, $y = |0\rangle$, get $|f(1)\rangle$

By linearity, if $x = \frac{|0\rangle + |1\rangle}{\sqrt{2}}$

we get

$$\frac{|0\rangle|f(0)\rangle + |1\rangle|f(1)\rangle}{\sqrt{2}}$$

Remarkable state!

Quantum Parallelism

n bits.

- Prepare $n+1$ qubit state $|0\rangle^{\otimes n} |0\rangle$
- Apply $H^{\otimes n}$ on first n bits.
- Apply quantum circuit implementing f
to get

$$\frac{1}{\sqrt{2^n}} \sum_{x \in \{0,1\}^n} |x\rangle |f(x)\rangle.$$